

CENG 3420

Computer Organization & Design



Lecture 07: Arithmetic and Logic Unit – 2

Bei Yu

CSE Department, CUHK

byu@cse.cuhk.edu.hk

(Latest update: January 20, 2022)

Spring 2022



Multiplication & Division




- More complicated than addition
- Can be accomplished via [shifting](#) and [adding](#)

$$\begin{array}{r} 0010 \quad (\text{multiplicand}) \\ \times 1011 \quad (\text{multiplier}) \\ \hline 0010 \\ 0010 \\ 0000 \\ 0010 \\ \hline 00010110 \quad (\text{product}) \end{array}$$


(partial product array)

- Double precision product produced
- More time and more area to compute

First Version of Multiplication Hardware

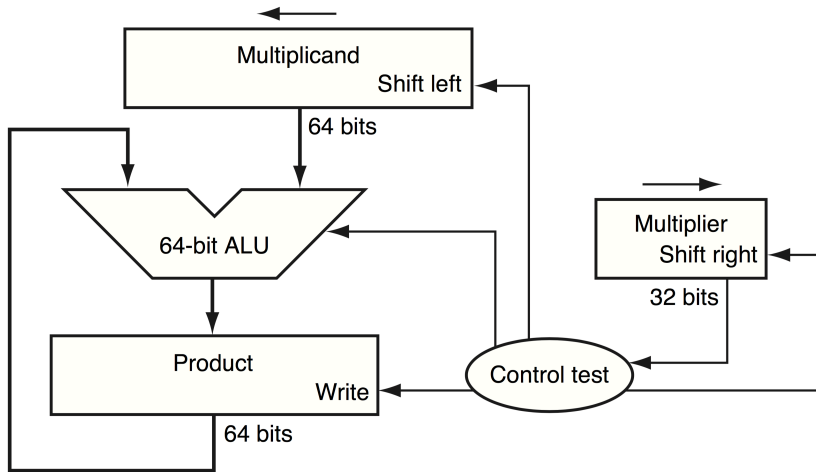

Add and Right Shift Multiplier Hardware

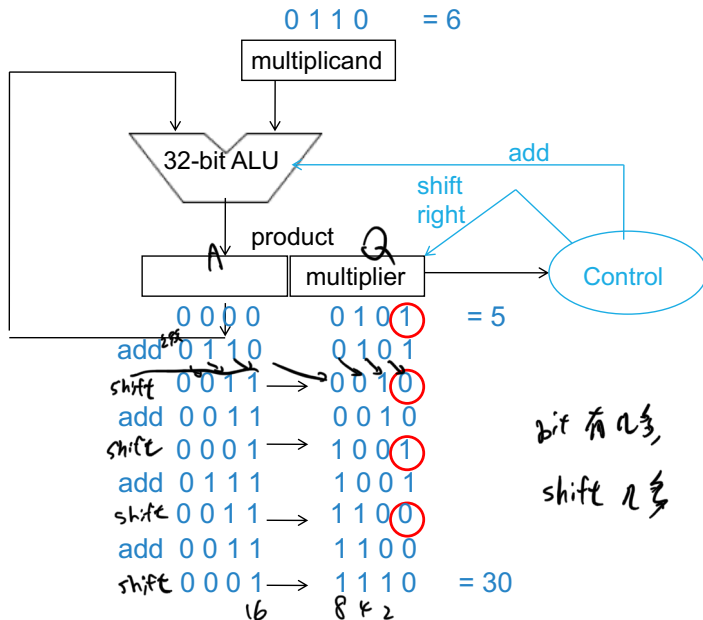



- Multiply (`mult` and `multu`) produces a double precision product


```
mul $rd, $s0, $s1      # hi/lo = $s0 * $s1
```

0	16	17	0	0	0x18
---	----	----	---	---	------

- Low-order word of the product is left in processor register `lo` and the high-order word is left in register `hi`
- Instructions `mfhi rd` and `mflo rd` are provided to move the product to (user accessible) registers in the register file
- Multiplies are usually done by fast, dedicated hardware and are much more complex (and slower) than adders



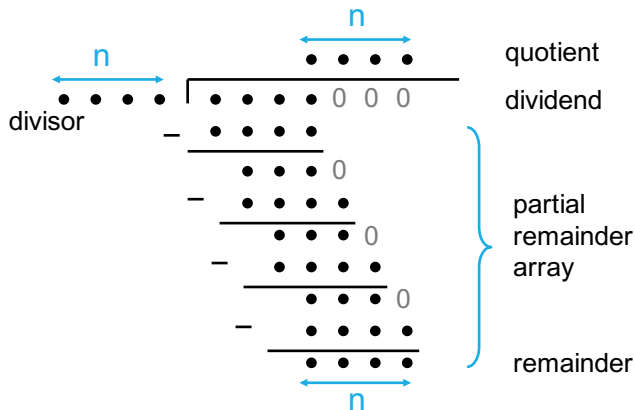- Division is just a bunch of quotient digit guesses and left shifts and subtracts





Question: Division

Dividing 1001010 by 1000

$$\begin{array}{r} 1001 \\ 1000 \overline{) 1001010} \\ \underline{1000} \\ 0010 \\ \underline{0000} \\ 0101 \\ \underline{1000} \\ 1010 \\ \underline{1000} \\ 10 \end{array}$$



- Divide generates the remainder in `hi` and the quotient in `lo`

```
div $rd, $s0, $s1      # lo = $s0 / $s1  
                        # hi = $s0 mod $s1
```

op	rs	rt	rd	shamt	funct
----	----	----	----	-------	-------

- Instructions `mflo rd` and `mfhi rd` are provided to move the quotient and remainder to (user accessible) registers in the register file
- As with multiply, divide ignores overflow so software must determine if the quotient is too large.
- Software must also check the divisor to avoid division by 0.



Shift



- Shifts move all the bits in a word left or right


```
sll    $t2, $s0, 8  # $t2 = $s0 << 8 bits
srl    $t2, $s0, 8  # $t2 = $s0 >> 8 bits
sra    $t2, $s0, 8  # $t2 = $s0 >> 8 bits
```


op	rs	rt	rd	shamt	funct
----	----	----	----	-------	-------

- Notice that a 5-bit `shamt` field is enough to shift a 32-bit value $2^5 - 1$ or 31 bit positions
- Logical shifts fill with **zeros**, arithmetic left shifts fill with the **sign bit**


The shift operation is implemented by hardware separate from the ALU

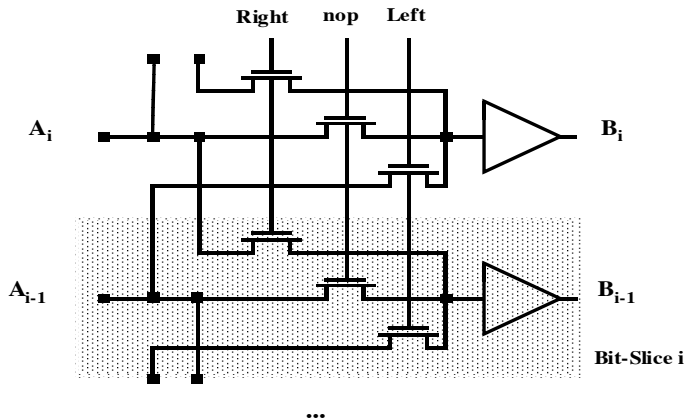Using a barrel shifter, which would takes lots of gates in discrete logic, but is pretty easy to implement in VLSI




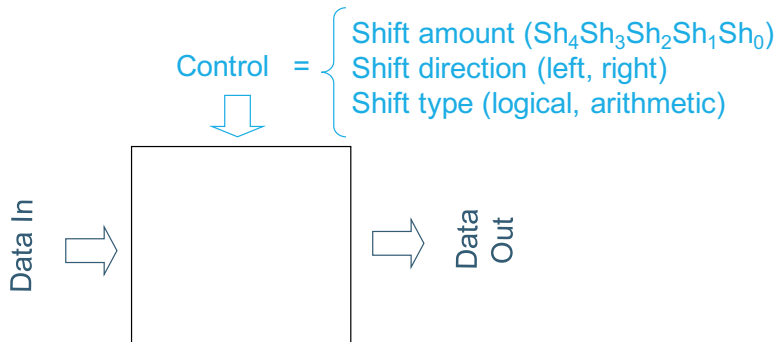


Logarithmic Shifter Structure

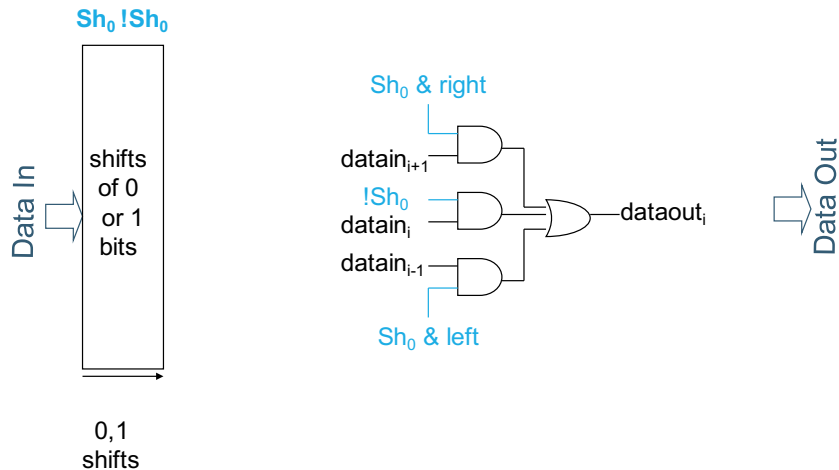


Logarithmic Shifter Structure

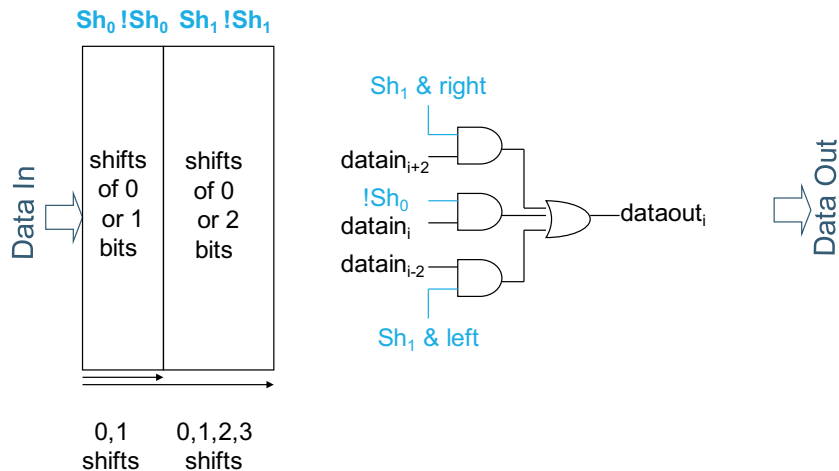


Logarithmic Shifter Structure

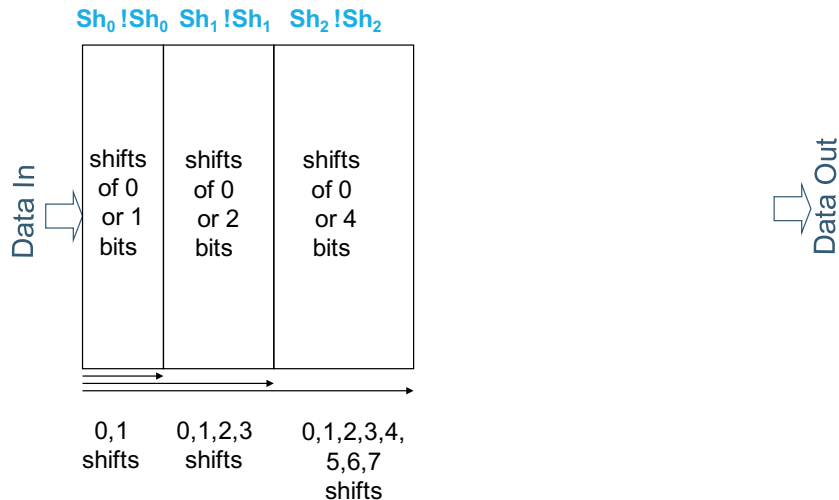

Logarithmic Shifter Structure

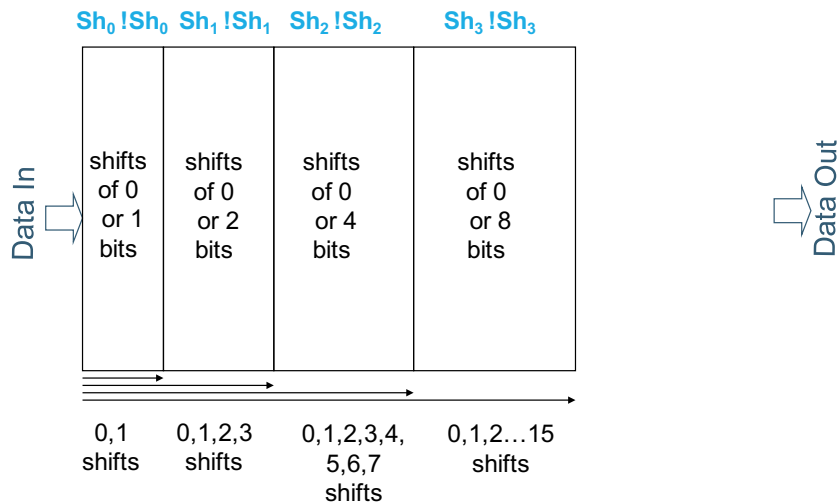

Logarithmic Shifter Structure

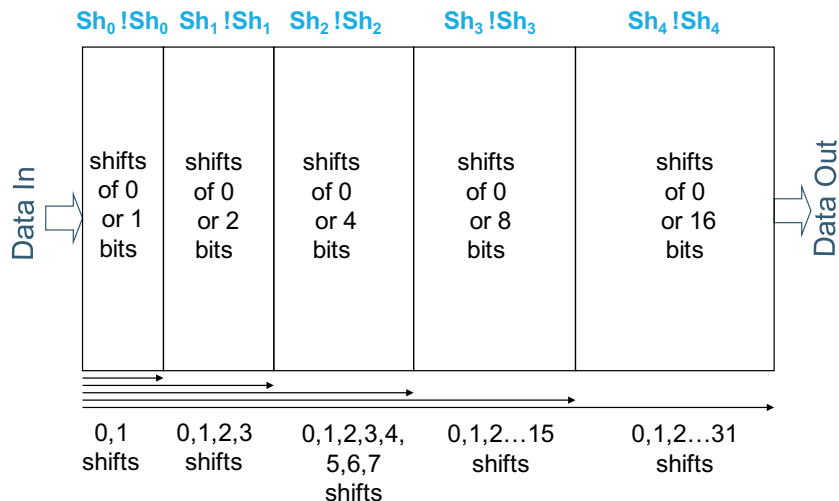

Logarithmic Shifter Structure

