CENG 3420
Computer Organization & Design

Lecture 11: Pipeline – Basis

Bei Yu
CSE Department, CUHK
byu@cse.cuhk.edu.hk

(Textbook: Chapters 4.5 & 4.6)

Spring 2022

Single Cycle Disadvantages

- Single cycle: the whole datapath is finished in one clock cycle
- It is simple and easy to understand
- Uses the clock cycle inefficiently – the clock cycle must be timed to accommodate the slowest instr
- Problematic for more complex instructions like floating point multiply
- May be wasteful of area since some functional units (e.g., adders) must be duplicated since they can not be shared during a clock cycle

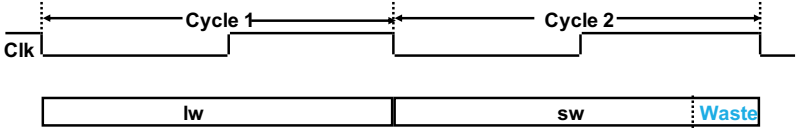

Single Cycle Disadvantages

- Though simple, the single cycle approach is not used because it is very slow
- Clock cycle must have the same length for every instruction
- What is the longest path (slowest instruction)? Load instruction!
- It is too long for the store instruction so the last part of the cycle here is wasted.

EX: Instruction Critical Paths

Calculate cycle time assuming negligible delays (for muxes, control unit, sign extend, PC access, shift left 2, wires) except:

- Instruction memory (IM) and data memory (DM) (4 ns)
- ALU and adders (ALU) (2 ns)
- Register File access (Reg) (1 ns)

Instr.	IM	Reg	ALU	DM	Reg	Total
R/I-type						
`lw`						
`sw`						
`beq`						
`jal`						
`jalr`						

EX: Instruction Critical Paths

Calculate cycle time assuming negligible delays (for muxes, control unit, sign extend, PC access, shift left 2, wires) except:

- Instruction memory (IM) and data memory (DM) (4 ns)
- ALU and adders (ALU) (2 ns)
- Register File access (Reg) (1 ns)

Instr.	IM	Reg	ALU	DM	Reg	Total
R/I-type	4	1	2		1	8
`lw`	4	1	2	4	1	12
`sw`	4	1	2	4		11
`beq`	4	1	2			7
`jal`						
`jalr`						

Solution:

Instr.	IM	Reg	ALU	DM	Reg	Total
R/I-type	4	1	2		1	8
`lw`	4	1	2	4	1	12
`sw`	4	1	2	4		11
`beq`	4	1	2			7
`jal`	4		2		1	7
`jalr`	4	1	2		1	8

How Can We Make It Faster?

$$\text{CPU time} = \text{CPI} \times \text{CC} \times \text{IC}$$

- Start fetching and executing the next instruction before the current one has completed
  - Pipelining – (all?) modern processors are pipelined for performance
  - Under ideal conditions and with a large number of instructions, the speedup from pipelining is approximately equal to the number of pipe stages
  - A five stage pipeline is nearly five times faster because the CC is "nearly" five times faster
- Fetch (and execute) more than one instruction at a time
  - Superscalar processing – stay tuned

Note:

- CC: clock cycle;
- IC: instruction count
- In reality the time per instruction in a pipeline processor is longer than the minimum possible because
  1. the pipeline stages may not be perfectly balanced
  2. pipelining involves some overhead (like pipeline stage isolation registers).

The Five Stages of Load Instruction

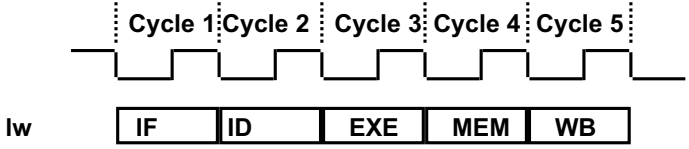

- IF: Instruction Fetch and Update PC
- ID: Registers Fetch and Instruction Decode
- EXE: Execute R-type; calculate memory address
- MEM: Read/write the data from/to the Data Memory
- WB: Write the result data into the register file

Equivalent Definitions

In this course, we treat the following definitions equivalent:

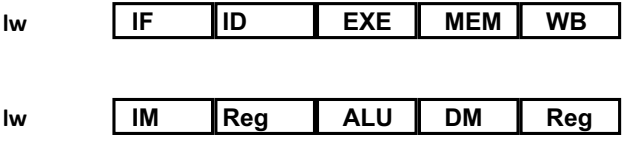

A Pipelined RISC-V Processor

Start the next instruction before the current one has completed

- improves throughput - total amount of work done in a given time
- instruction latency (execution time, delay time, response time - time from the start of an instruction to its completion) is not reduced

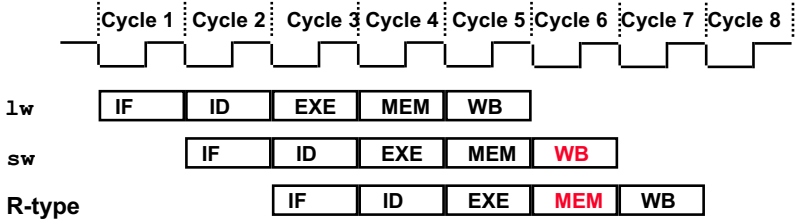

1. clock cycle (pipeline stage time) is limited by the slowest stage
2. for some stages don't need the whole clock cycle (e.g., WB)
3. for some instructions, some stages are wasted cycles (i.e., nothing is done during that cycle for that instruction)

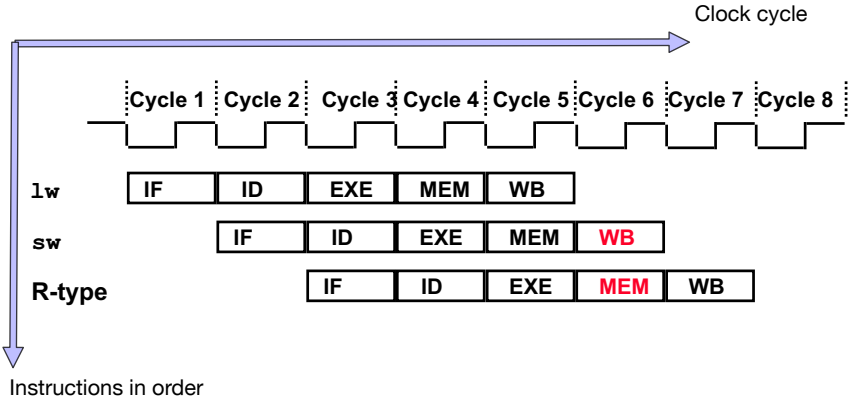
Clock cycle
Cycle 1
Cycle 2
Cycle 3
Cycle 4
Cycle 5
Cycle 6
Cycle 7
Cycle 8
lw
IF
ID
EXE
MEM
WB
sw
IF
ID
EXE
MEM
WB
R-type
IF
ID
EXE
MEM
WB
Instructions in order

Single Cycle versus Pipeline

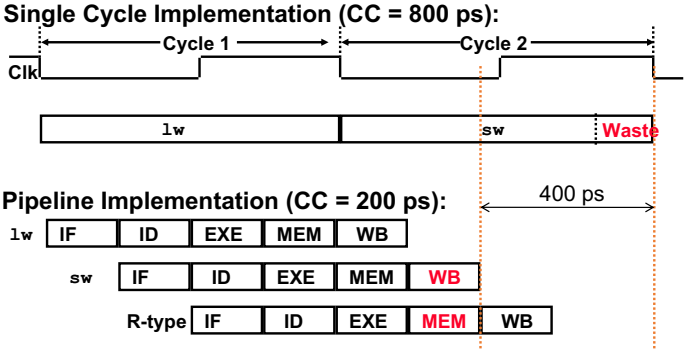

- To complete an entire instruction in the pipelined case takes 1000 ps (as compared to 800 ps for the single cycle case). Why ?
- How long does each take to complete 1,000,000 adds ?

Example:

If IF=100ps, ID=100ps, EXE=200ps, MEM=200ps, WB=100ps

- In single cycle setting, cycle-length=700ps
- In pipeline setting, each cycle length=200ps, so finish one instr will take 5 stages (ie. 5×200ps).

What makes it easy

- all instructions are the same length (32 bits)
  - can fetch in the 1st stage and decode in the 2nd stage
- few instruction formats (three) with symmetry across formats
  - can begin reading register file in 2nd stage
- memory operations occur only in loads and stores
  - can use the execute stage to calculate memory addresses
- each instruction writes at most one result (i.e., changes the machine state) and does it in the last few pipeline stages (MEM or WB)
- operands must be aligned in memory so a single data transfer takes only one data memory access

RISC-V Pipeline Datapath Additions/Mods

State registers between each pipeline stage to isolate them

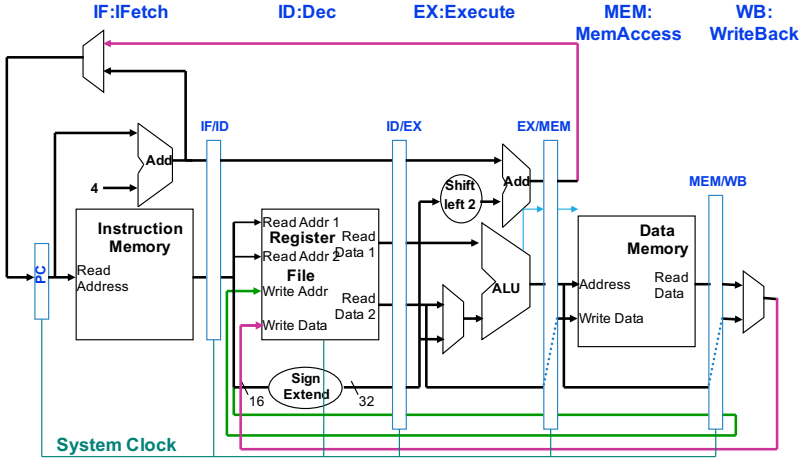

RISC-V Pipeline Control Path Modifications

All control signals can be determined during Decode

- and held in the state registers between pipeline stages

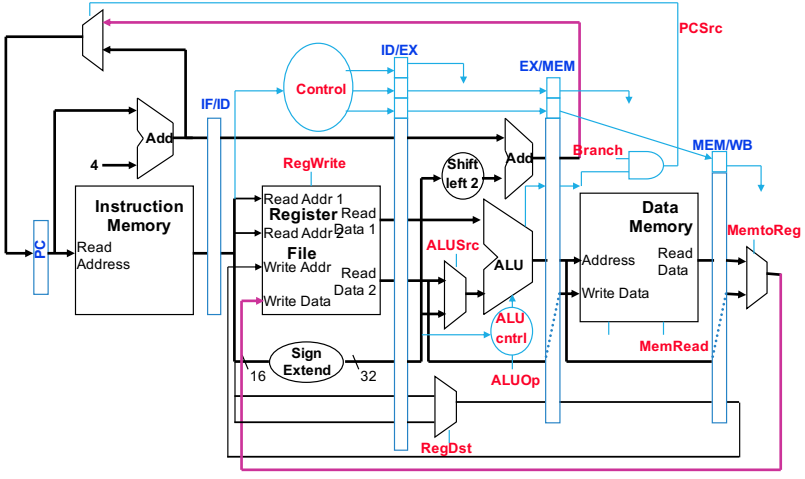

Pipeline Control

- IF Stage: read Instr Memory (always asserted) and write PC (on System Clock)
- ID Stage: no optional control signals to set

	EX Stage				MEM Stage			WB Stage	
	Reg Dst	ALU Op1	ALU Op0	ALU Src	Brch	Mem Read	Mem Write	Reg Write	Mem toReg
R	1	1	0	0	0	0	0	1	0
`lw`	0	0	0	1	0	1	0	1	1
`sw`	X	0	0	1	0	0	1	0	X
`beq`	X	0	1	0	1	0	0	0	X

Graphically Representing RISC-V Pipeline

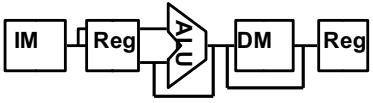

Can help with answering questions like:

- How many cycles does it take to execute this code?
- What is the ALU doing during cycle 4?
- Is there a hazard, why does it occur, and how can it be fixed?

Other Pipeline Structures Are Possible

What about the (slow) multiply operation?

- Make the clock twice as slow or ...
- let it take two cycles (since it doesn't use the DM stage)

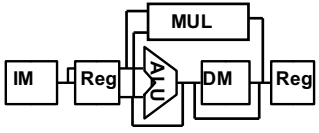

What if the data memory access is twice as slow as the instruction memory?

- make the clock twice as slow or ...
- let data memory access take two cycles (and keep the same clock rate)

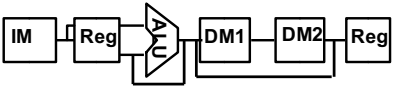

Other Sample Pipeline Alternatives

- ARM7:

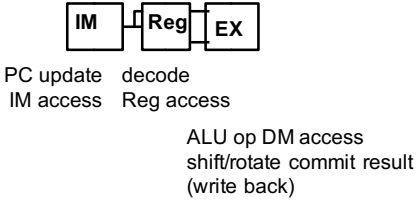

- XScale:

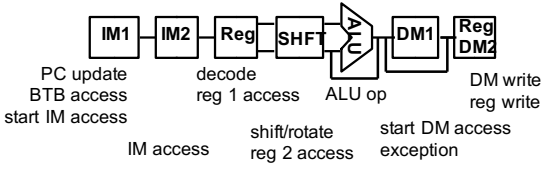

Why Pipeline? For Performance!

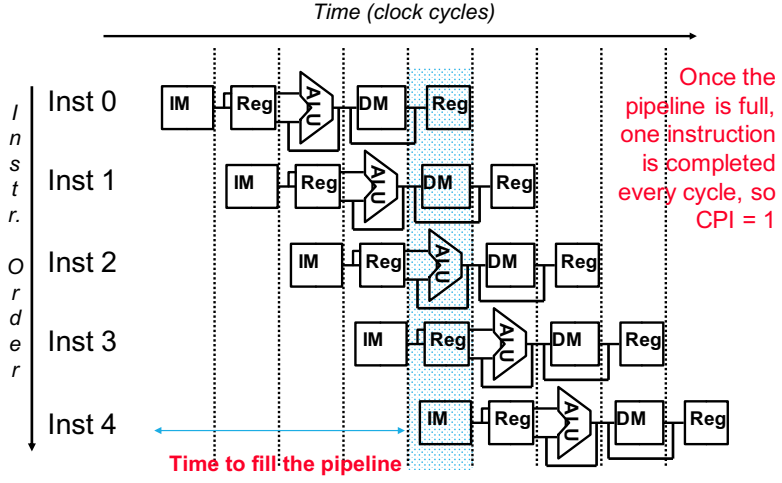

Can Pipelining Get Us Into Trouble?

Yes! Pipeline Hazards

- structural hazards: a required resource is busy
- data hazards: attempt to use data before it is ready
- control hazards: deciding on control action depends on previous instruction

Can usually resolve hazards by waiting

- pipeline control must **detect** the hazard
- and take action to **resolve** hazards

Structure Hazards

- Conflict for use of a resource
- In RISC-V pipeline with a single memory
  - Load/store requires data access
  - Instruction fetch requires instruction access
- Hence, pipeline datapaths require separate instruction/data memories
  - Or separate instruction/data caches
- Since Register File

Resolve Structural Hazard 1

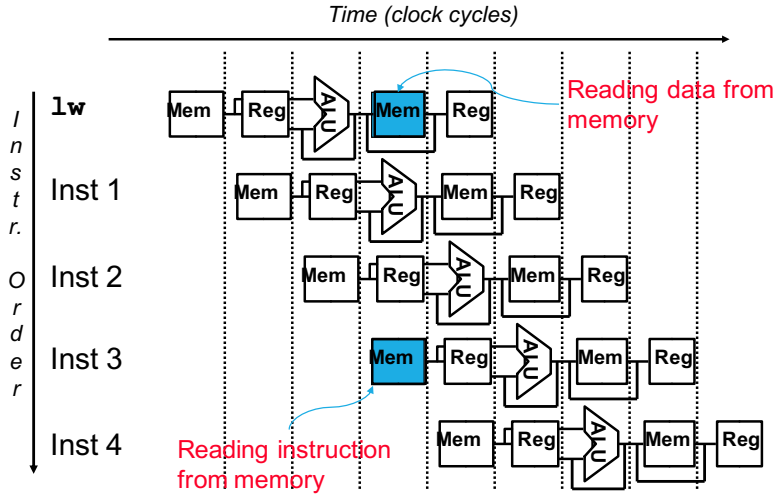

Fix with separate instr and data memories (I$ and D$)

Resolve Structural Hazard 2